

## DOD Overdrive 250

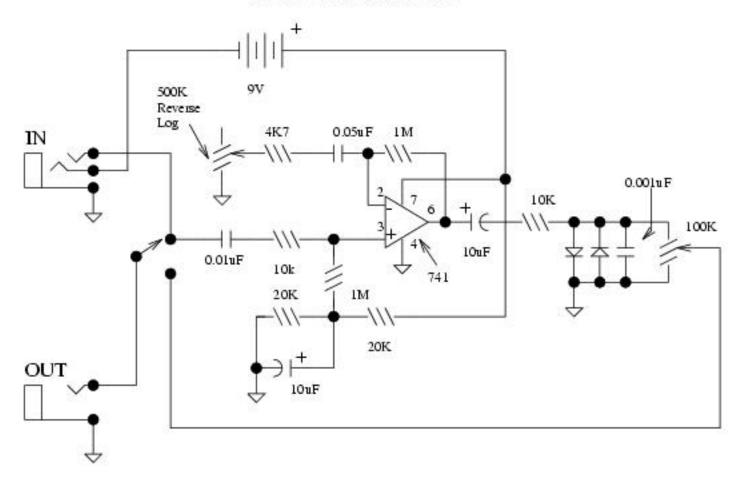


The DOD Overdrive 250 is Yet Another 741With Two Diodes On The Output. It is almost exactly the same as the MXR Distortion Plus, and a number of other units.


## DOD Compressor 280A

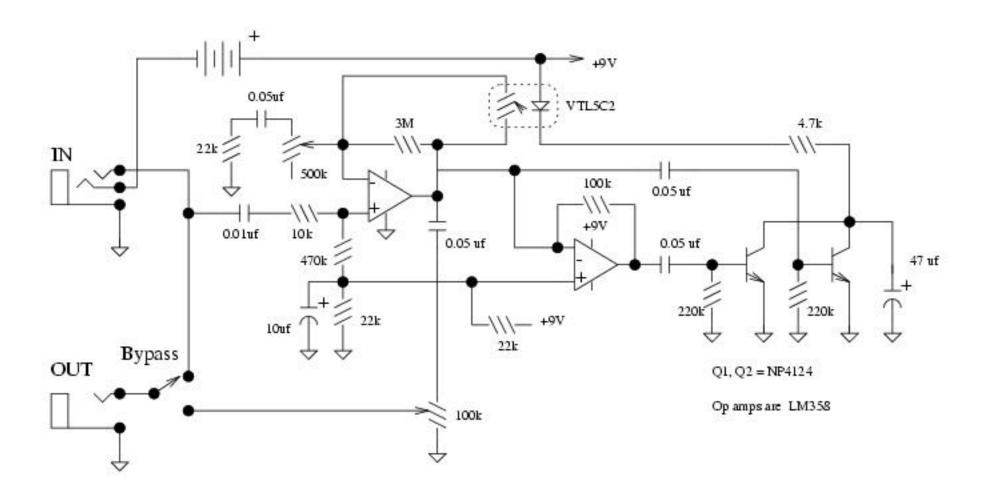

This is the original schematic, but it looks funny to me. I think that there should be a 100k resistor at the (-) input of the second opamp to make it a pure inverter. As it is, that stage would have a very large voltage gain, unbalancing what I think works as a full wave rectifier/current source for the LED in the compression feedback loop. I would expect that the proper circuit is as shown in the fragment below. I think the VTL5C2 LED/LDR module could be replaced with a CLM6000 if you could find one of those.

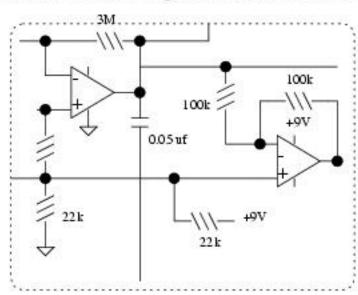

## DOD Envelope Filter 440

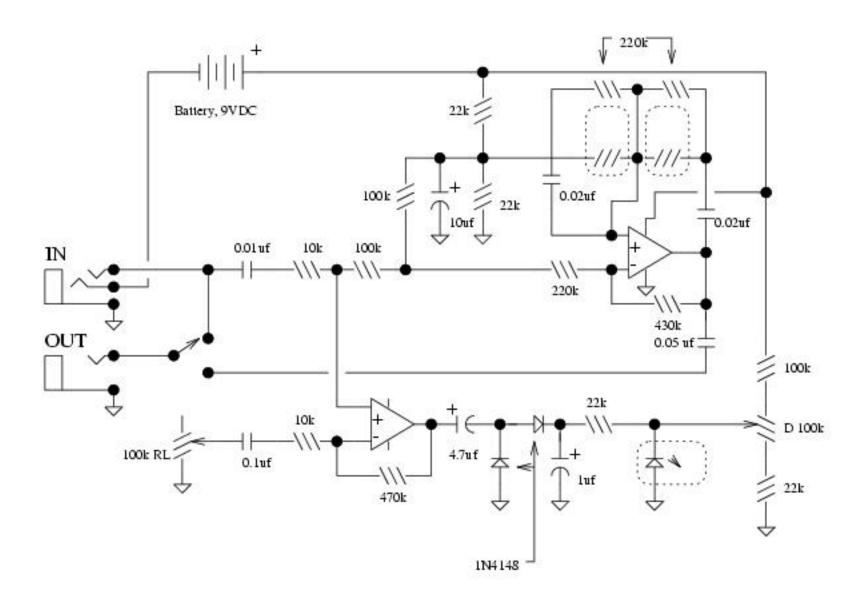

Opamps are each 1/2 of TL022dual low power opamp. LED/LDR module is unknown, but is probably a Vactec VTL module with LED to center-tapped LDR.

